

The accelerometer outputs a raw signal ranging from 700 mV to 2.2 V (with a 1.5 V swing). To output a 0 V – 5 V signal, the LM6144 Quad Op-Amp in an inverting configuration is used to amplify and center the signal on 2.5 V using a reference voltage. We see that a 3.3 gain is necessary. We will use the following equation to solve for the reference voltage.

$$V_{out} = (V_{ref} - V_{in}) * ((R_f / (R_i)) + V_{ref})$$

From the gain calculation we choose the following resistor values

$$R_f = 3.3 \text{ K}$$

$$R_i = 1 \text{ K}$$

We now fill in the equation with Vout as 5 V and Vin as .700 V

$$5 = (V_{ref} - .7) * (3.3\text{K}/1\text{K}) + V_{ref}$$

$$V_{ref} = 1.7 \text{ V}$$

The same calculation can be done with a Vout of 0 and Vin of 2.2

$$0 = (V_{ref} - 2.2) * (3.3\text{K}/1\text{K}) + V_{ref}$$

$$V_{ref} = 1.7 \text{ V}$$

We now can use a voltage divider to obtain the reference voltage.

$$V_{out} = V_{in} * (R_2 / (R_1 + R_2))$$

The flex sensor used for the throttle outputs a raw signal ranging from 1.36 V to 2.42 V (with a 1.06 V swing). To output a 0 V – 5 V signal, the LM6144 Quad Op-Amp in an inverting configuration is used to amplify and center the signal on 2.5 V using a reference voltage. We see that a 4.7 gain is necessary. We will use the following equation to solve for the reference voltage.

$$V_{out} = (V_{ref} - V_{in}) * ((R_f / (R_i)) + V_{ref})$$

From the gain calculation we choose the following resistor values

$$R_f = 47 \text{ K}$$

$$R_i = 10 \text{ K}$$

We now fill in the equation with Vout as 5 V and Vin as .700 V

$$5 = (V_{ref} - 1.36) * (47\text{K}/10\text{K}) + V_{ref}$$

$$V_{ref} = 2.2 \text{ V}$$

The same calculation can be done with a Vout of 0 and Vin of 2.2

$$0 = (V_{ref} - 2.42) * (47\text{K}/10\text{K}) + V_{ref}$$

$$V_{ref} = 2.2 \text{ V}$$

We now can use a voltage divider to obtain the reference voltage.

$$V_{out} = V_{in} * (R_2 / (R_1 + R_2))$$

Current Calculations

Component / Device	Max Current Draw
XBee	100 mA
Accelerometer	600 uA
Flex Sensor	250 uA
OpAmp	880 uA
Hall Switch	1.20 mA
MOSFET+ LED chain	300 mA
L7805 Quiescent Current	6 mA
Total	409 mA

Total battery capacity for NiCad batteries is 1500mA-h.

If all the subsystems run continuously, we need 3 batteries in parallel to meet the 8-hour control running time. Three batteries give us the capacity to run the controller for 11 hours. We are not running all the subsystems continuously. (The LEDs are off approximately $\frac{1}{4}$ of the time dropping our current consumption significantly.) Thus, 2 batteries are sufficient for 8 hours of running time.